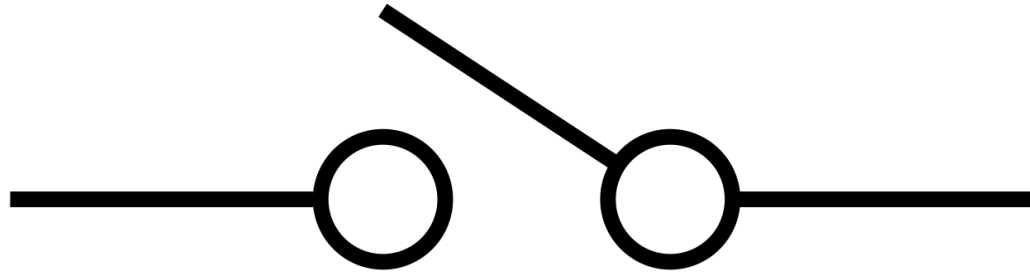


Digital Input

Read digital signals with Arduino Pin


Digital Inputs





Tactile Switch




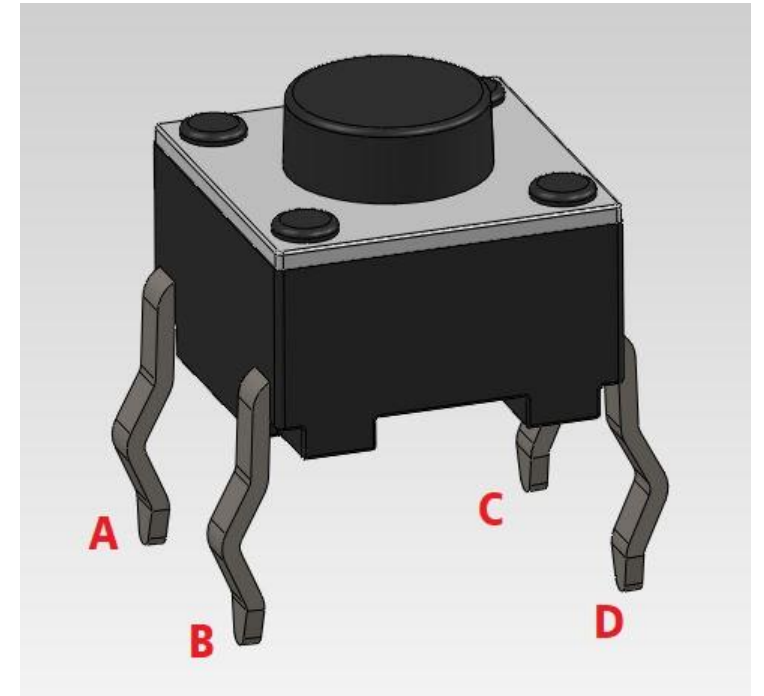
Pin A is ===== Pin B SHORT
Pin C is ===== Pin D SHORT



Pull Down

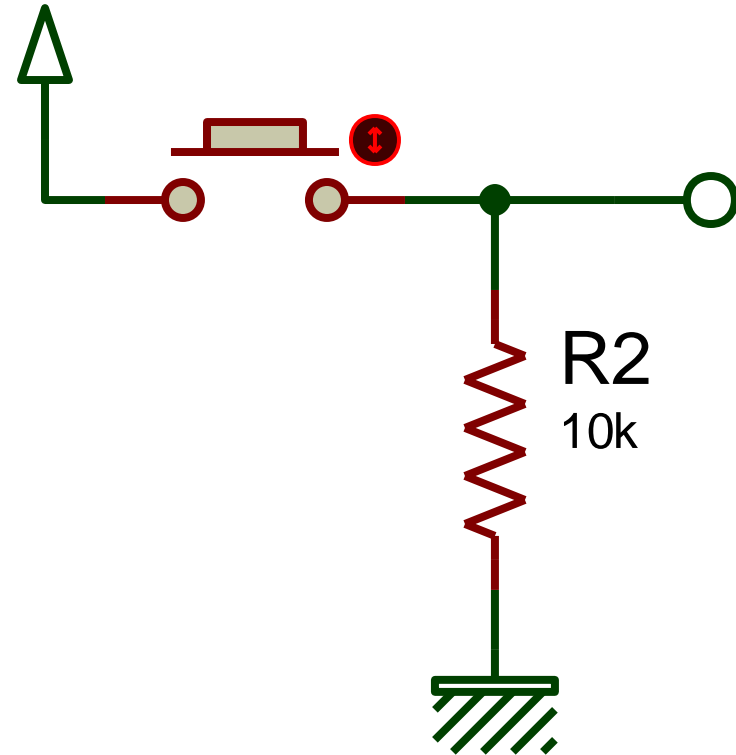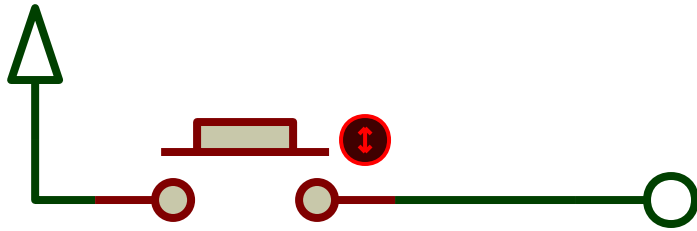

Pull Up

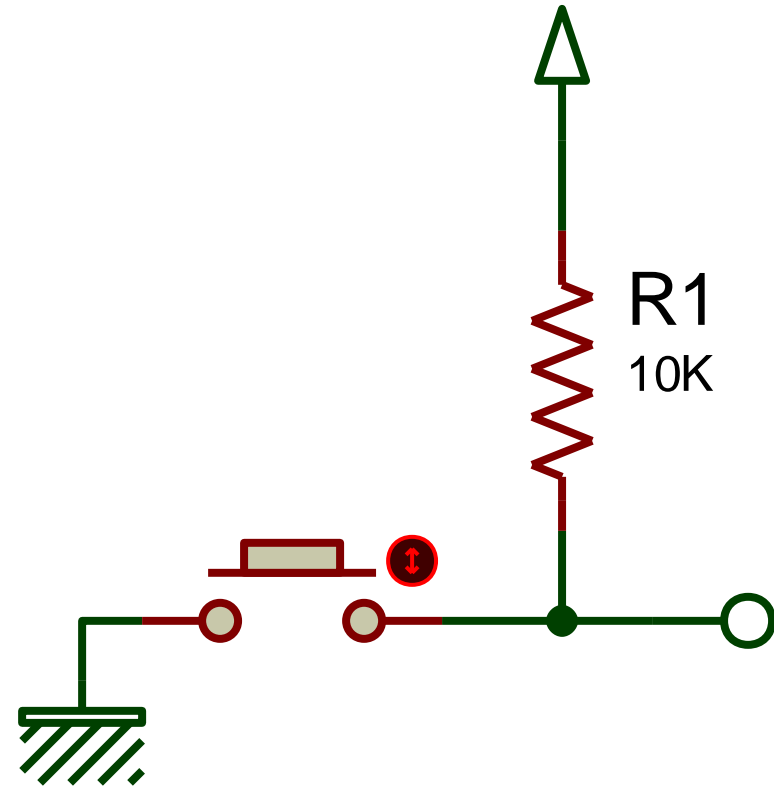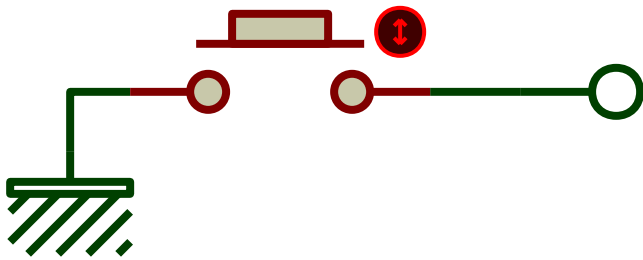

Digital Input


```
pinMode(pin number, INPUT);
```

```
pinMode(pin number, INPUT_PULLUP);
```

```
If(digital Read(2) == LOW)
```


```
If(digital Read(2) == HIGH)
```

Interfacing With Arduino, pull Down

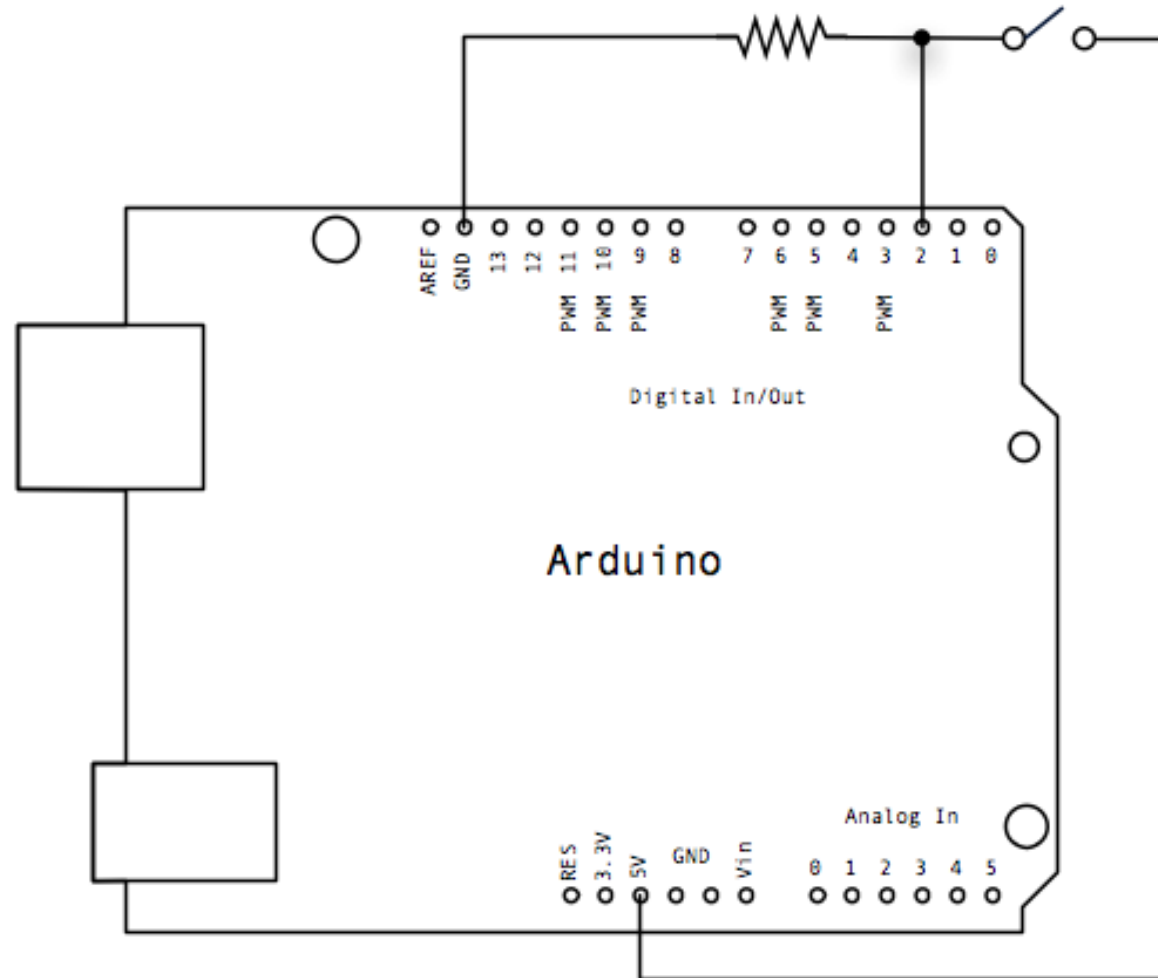

Project

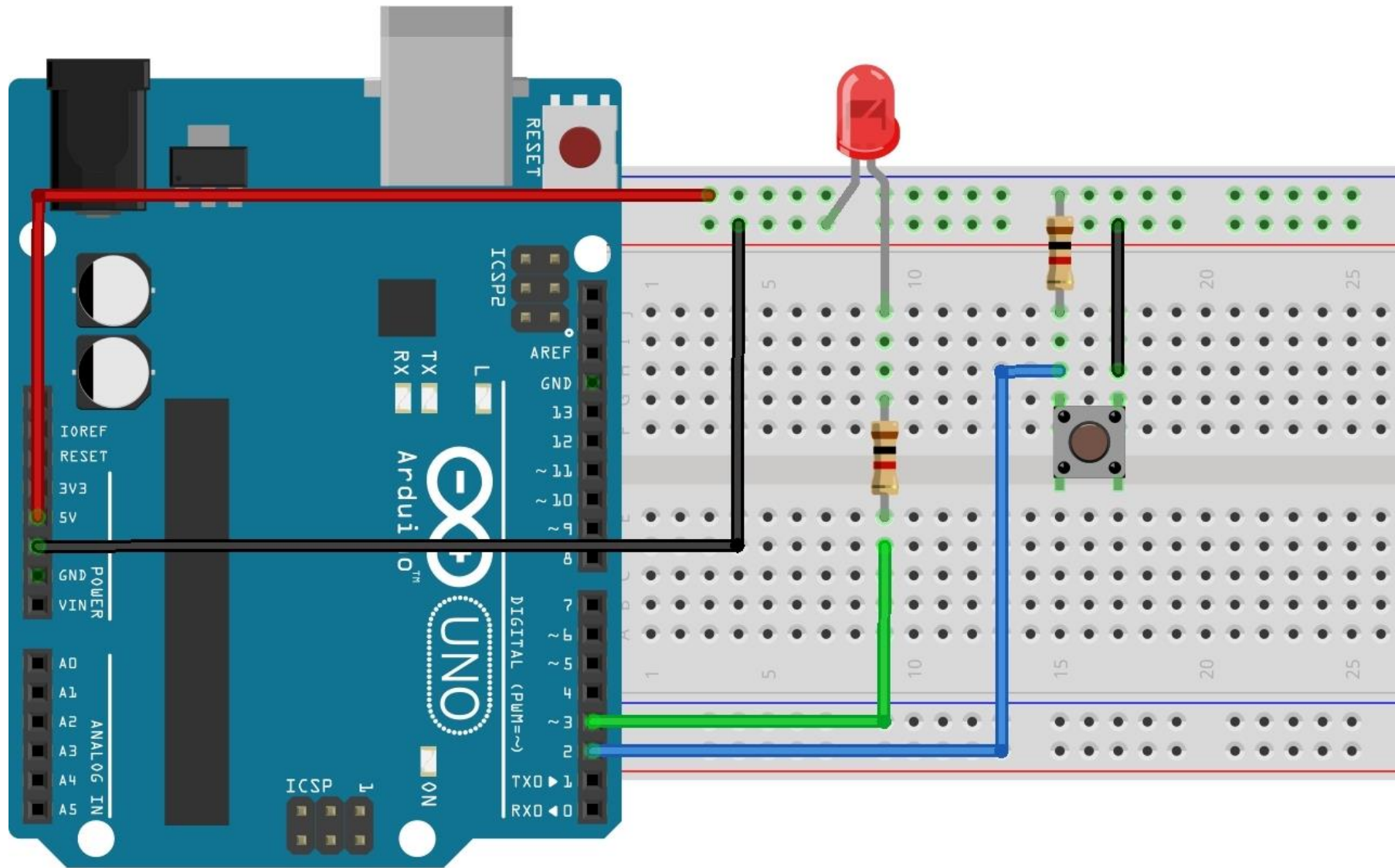- connect a switch to arduino pin 2
- connect other point of switch to vcc
- connect a pull down resistor
- use an LED at pin 13
- if switch is pressed, LED will turn ON,
- if switch is not pressed, LED will turn OFF



Code

```
led = 13;
sw = 2;
void setup()
{
    pinMode(sw, INPUT);
    pinMode(led, OUTPUT);
}
void loop()
{
    if(digitalRead(sw) == HIGH)
    {
        digitalWrite(led, HIGH);
    }
    else
    {
        digitalWrite(led, LOW);
    }
}
```

Built-in Pullup resistor in Arduino

- Every pin of Arduino has a built-in pullup resistor
- Pulls the pin to high

`pinMode(sw,INPUT_PULLUP);` OR




`pinMode(sw,INPUT);`

`digitalWrite(sw,HIGH);`

Use the switch against GND in this configuration and the code will also reverse

Using Digital Output Sensors

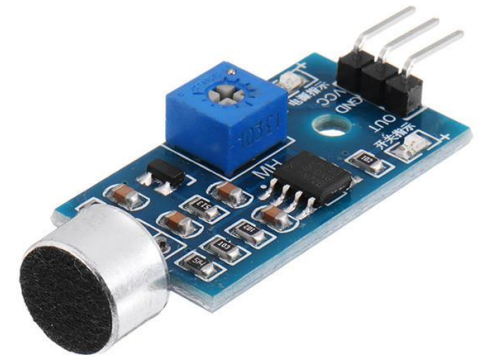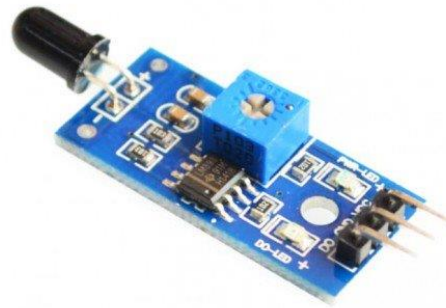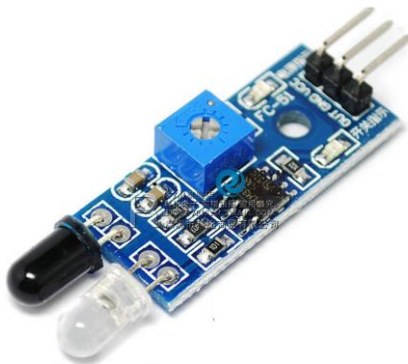- You can use digital Output sensors directly with Arduino
- No need to enable / connect external pull Up or Down
- Sensor takes care of it



Tasks

- Interface one switch and one LED, led on when switch pressed and led off when switch is released
- 2 switches and 2 LED's, when switch is pressed, both leds on, when switch 2 is pressed, both leds off
- When switch 1 is pressed, both led's blink 5 times, when switch 2 is pressed, both LEDs will blink 15 times