


# Light Emitting Diode



Light


Emitting

Diode

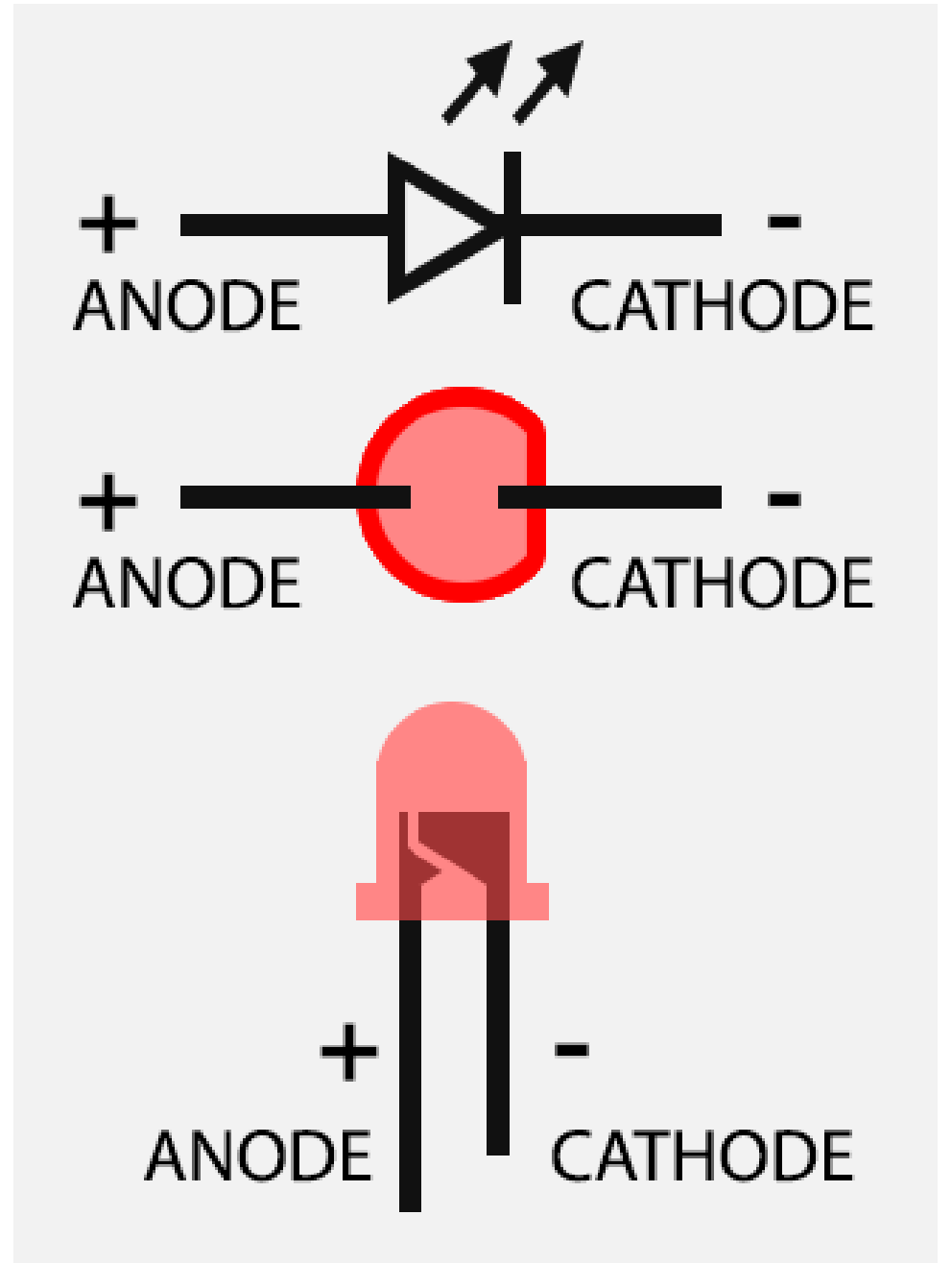
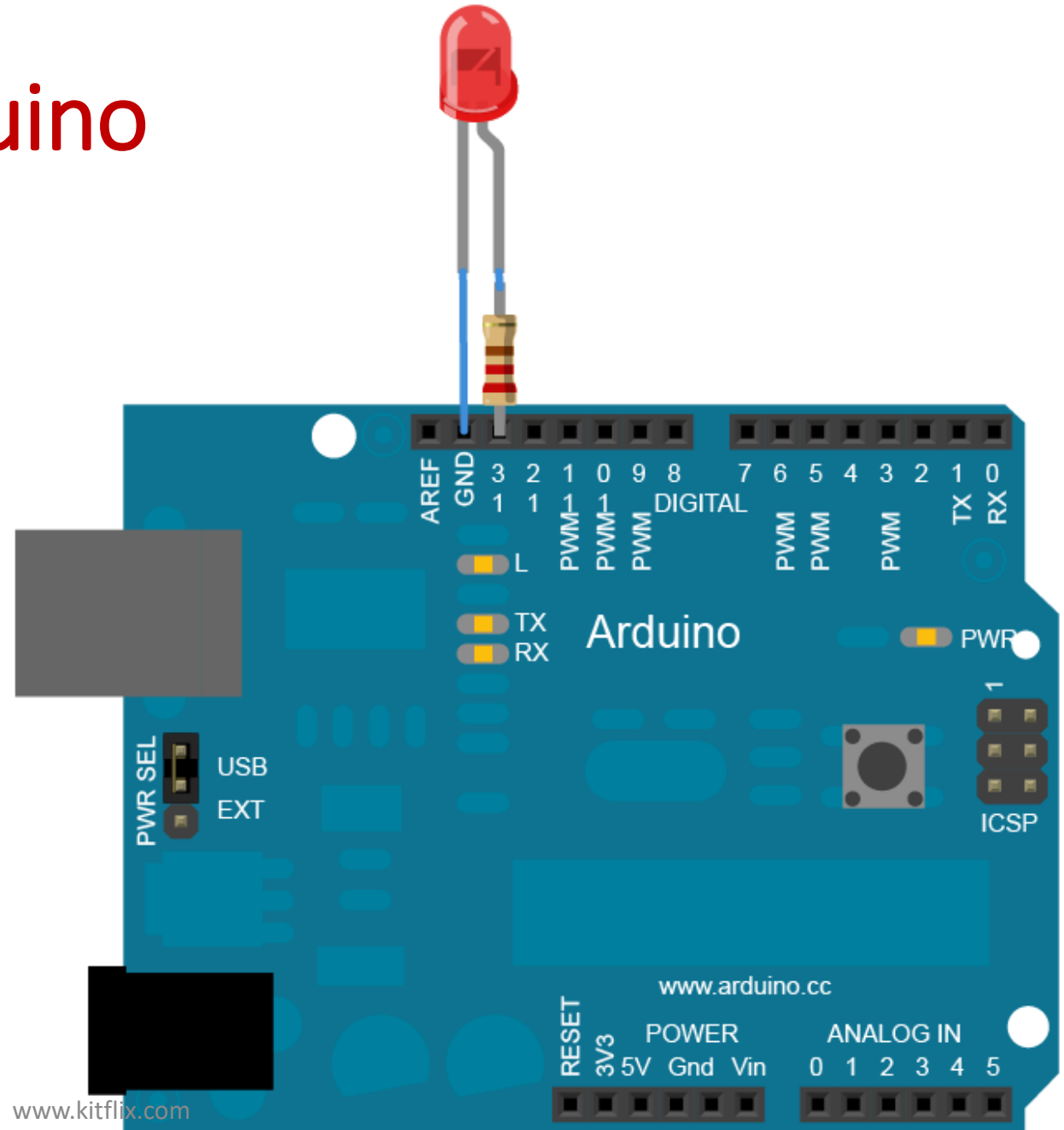
# Interfacing With Arduino

- Every Arduino has an LED on Pin no 13
- While connecting LED, ensure to use at least 100 ohm or more value resistor with LED
- Small LED's require 5mA to 50mA of current
- Job is just indication not lighting 😊00




# Digital Output

```
digitalWrite(13, HIGH);
```

```
digitalWrite(13, LOW);
```

# 8 x LEDs with Arduino

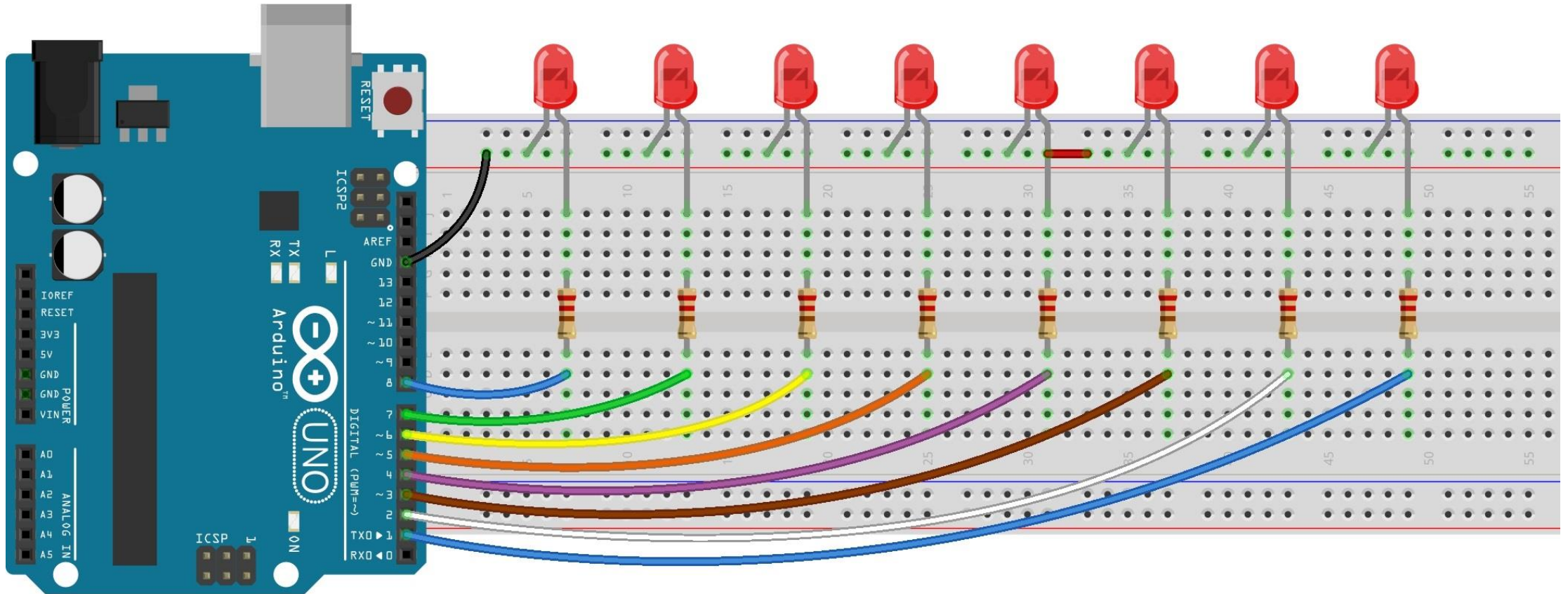

# Projects

- Interface 8 LEDs to an Aduino and Blink All 8 LED's On and Off
- Write down a code to make 4 LED's On and other 4 Off, and then first 4 Off and the later 4 on
- Chaser, Only one LED on, rest off
- Write a program to make LEDs turn on / off only 10 time

# Tri Color Led




**1 - RED**  
**2 - GROUND**  
**3 - GREEN**  
**4 - BLUE**



**1 - RED**  
**2 - +5V**  
**3 - GREEN**  
**4 - BLUE**

# Interfacing With Arduino

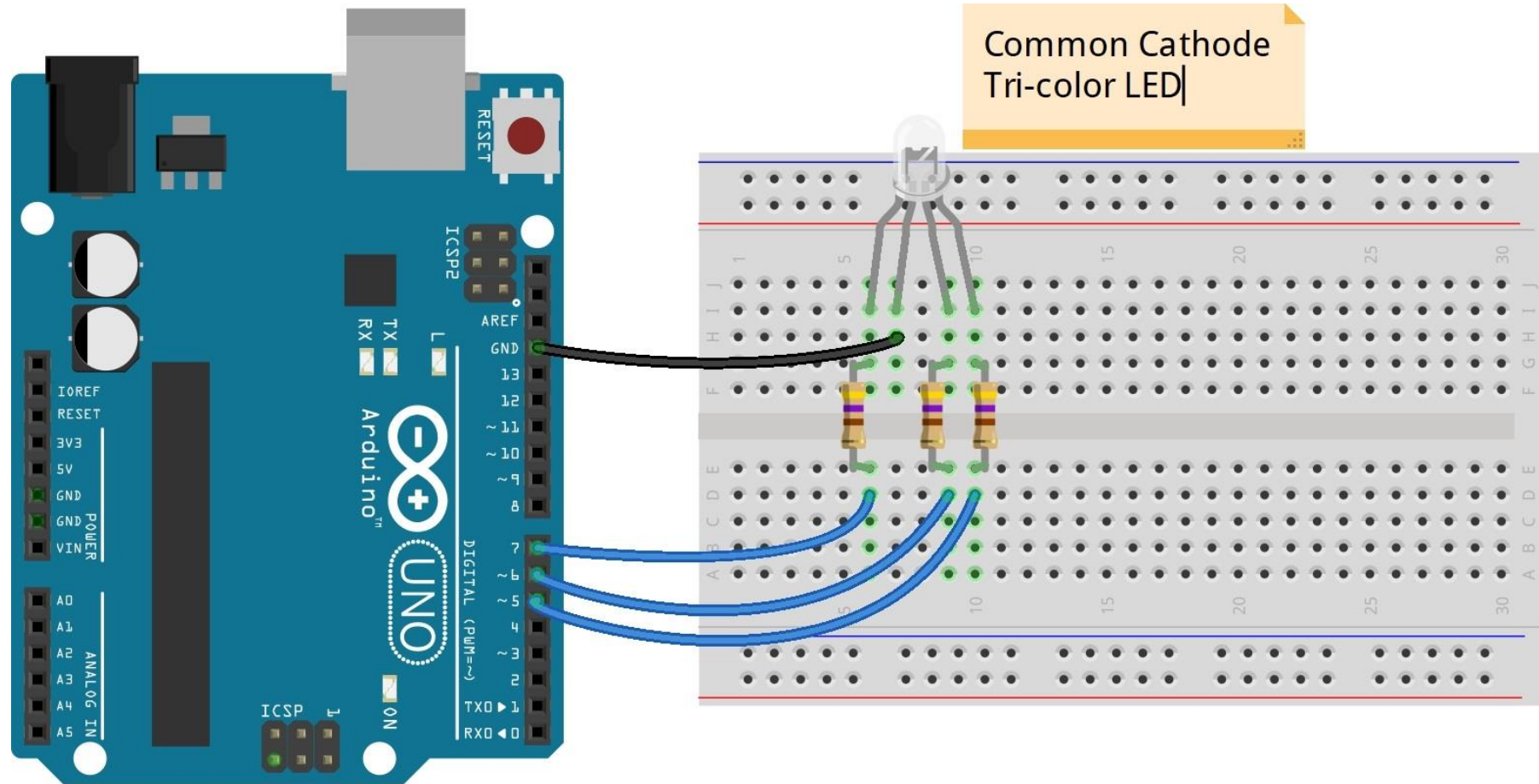



# Projects

- Automatic Traffic Signal with Tricolor LED
- 3 Switches and 3 LED's to generate red / green / blue when corresponding switch is pressed